

ELECTRONICS II

School of EE-ECE-COE
Mapua Institute of Technology

1

Course Content

- # Small-Signal BJT Amplifiers
- # Power Amplifiers
- # Field-Effect Transistor Biasing
- # Small-Signal FET Amplifiers
- # Amplifier Frequency Response
- # General Feedback Theory


2

Intro to Small-Signal Amplifiers

- # The Q-point of a transistor is set by dc biasing
- # Small-signal amplifiers are designed to handle small ac signals that cause relatively small variations about the Q-point.
- # Convention used for dc and ac values:
 - dc values, e.g. I_E , R_E
 - ac values, e.g. I_e (rms is assumed unless otherwise stated), R_e , r'_e (internal r of t' istor)
 - instantaneous values, e.g. i_e

3

Basic Small-Signal Amplifier

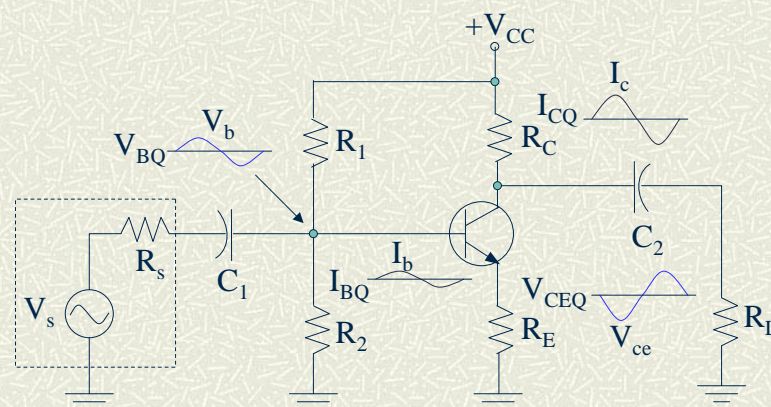

C_1 and C_2 block dc voltage but pass ac signal.


4

Small-Signal Amplifier Operation

- # Coupling capacitors C_1 and C_2 prevent R_s and R_L from changing the dc bias voltages
- # V_s causes V_b and I_b to vary slightly which in turn produces large variations in I_c due to β
- # As I_c increases, V_{ce} decreases and vice versa
- # Thus, V_c (output to R_L) is 180° out of phase with V_b

5

Graphical Picture

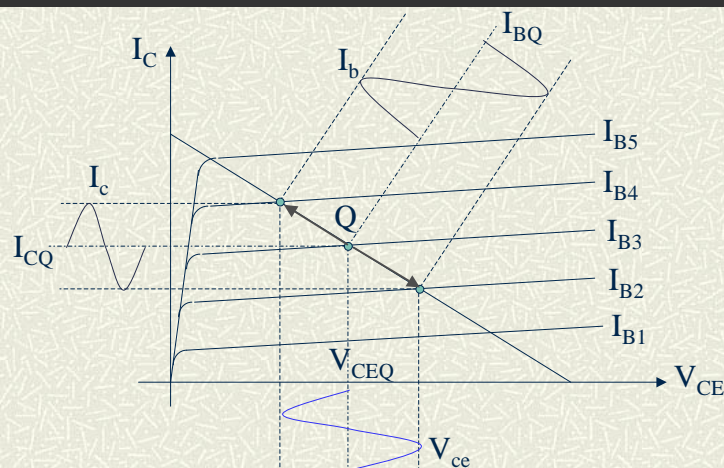

6

h Parameters

- # *h* (hybrid) parameters are typically specified on a manufacturer's data sheet.
 - h_i : input resistance; output shorted
 - h_r : voltage feedback ratio, input open
 - h_f : forward current gain; output shorted
 - h_o : output conductance; input open
- # Each *h* parameter has a 2nd subscript letter to designate configuration, e.g. h_{fe} , h_{fc} , h_{fb}

7

Amplifier Configurations

- # Common-emitter amplifier: emitter is connected to ground, input is applied to base, and output is on collector
- # Common-collector: collector is grounded, input is at base, and output is on emitter
- # Common-base: base is grounded, input is at emitter, and output is on collector

8

h-parameter Ratios

Common-Emitter Common-Base Common-Collector

$$h_{ie} = V_b/I_b \quad h_{ib} = V_e/I_b \quad h_{ic} = V_b/I_b$$


$$h_{re} = V_b/V_c \quad h_{rb} = V_e/V_c \quad h_{rc} = V_b/V_e$$

$$h_{fe} = I_c/I_b \quad h_{fb} = I_c/I_e \quad h_{fc} = I_e/I_b$$

$$h_{oe} = I_c/V_c \quad h_{ob} = I_c/V_c \quad h_{oc} = I_e/V_e$$

9

h-parameter Equivalent Circuit

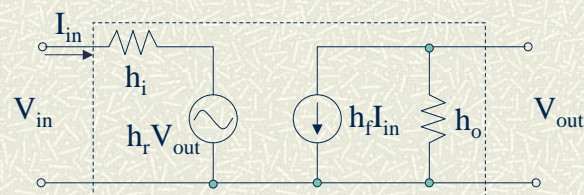

- # The above diagram is the general form of the *h*-parameter equivalent circuit for a BJT.
- # For the three different amplifier configurations, just add the appropriate second subscript letter.

10

r Parameters

The resistance, r , parameters are perhaps easier to work with

- α_{ac} : ac alpha (I_c/I_e)
- β_{ac} : ac beta (I_c/I_b)
- r_e' : ac emitter resistance
- r_b' : ac base resistance
- r_c' : ac collector resistance

Relationships of h and r parameters:


$$\alpha_{ac} = h_{fb} ; \beta_{ac} = h_{fe}$$

$$r_e' = \frac{h_{re}}{h_{oe}} ; r_c' = \frac{h_{re} + 1}{h_{oe}}$$

$$r_b' = h_{ie} - \frac{h_{re}}{h_{oe}}(1 + h_{fe})$$

11

r -Parameter Equivalent Circuits

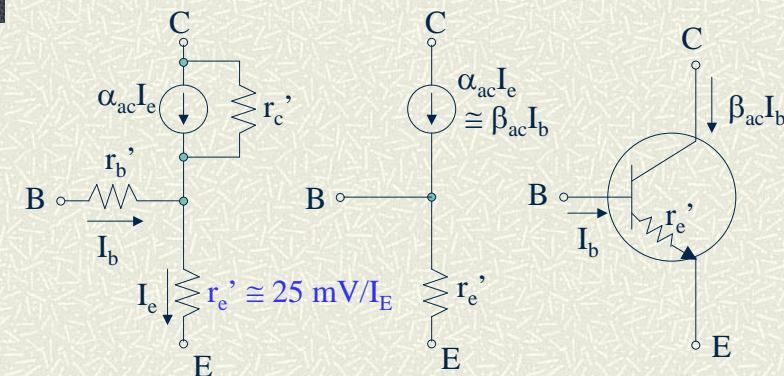


Generalized r -parameter equivalent circuit for BJT

Simplified r -parameter equivalent circuit and symbol of BJT

12


Difference between β_{ac} and β_{DC}

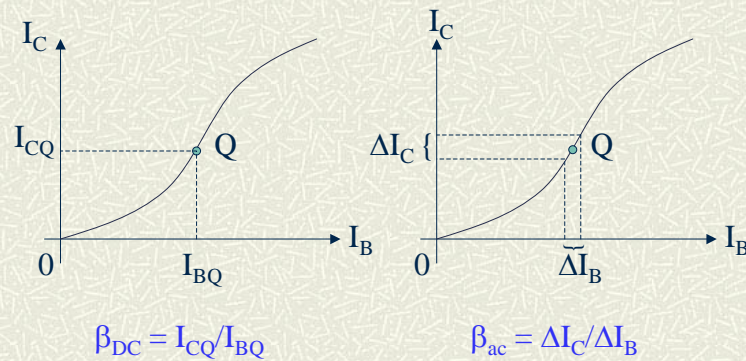

β_{DC} and β_{ac} values will generally not be identical and they also vary with the Q-point chosen.


13

Common-Emitter Amplifier

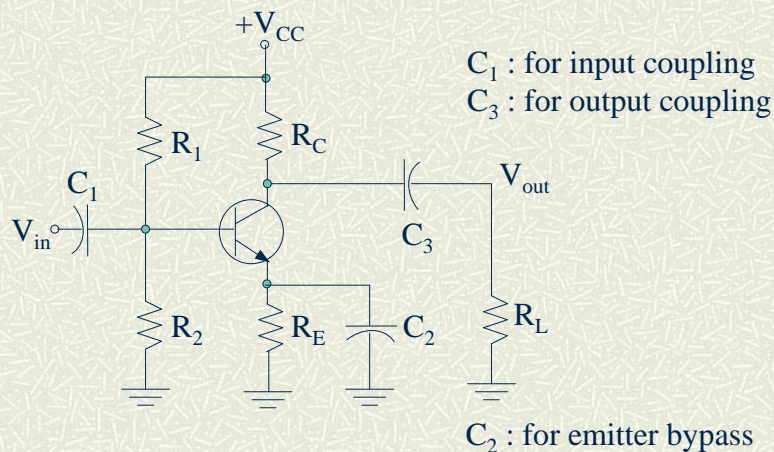

14

DC Analysis of CE Amplifier

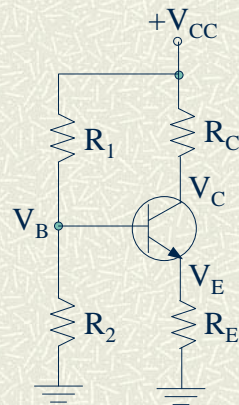

$$V_B = \left(\frac{R_2 // \beta_{DC} R_E}{R_1 + R_2 // \beta_{DC} R_E} \right) V_{CC}$$

If $\beta_{DC} R_E = R_{IN(base)} \gg 10R_2$, then


$$V_B \cong \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}$$

$$V_E = V_B - V_{BE}; \quad I_C \cong I_E = \frac{V_E}{R_E}$$

$$V_C = V_{CC} - I_C R_C$$

15

AC Analysis of CE Amplifier

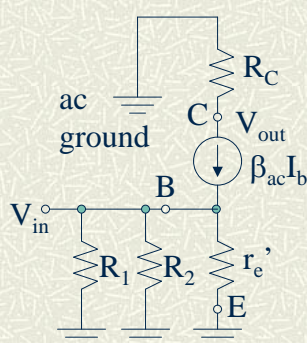

C_1 , C_2 , and C_3 are replaced by shorts assuming $X_C \cong 0$

Input and output resistance:

$$R_{in(tot)} = R_1 // R_2 // R_{in(base)}$$

$$\text{where } R_{in(base)} = \beta_{ac} r_e'$$

$$R_{out} \cong R_C \text{ (not including } R_L \text{)}$$

Voltage gain of CE amplifier:


$$A_v = \frac{V_{out}}{V_{in}} = \frac{V_c}{V_b} = \frac{-I_c R_C}{I_e r_e'} = -\frac{R_C}{r_e'}$$

If R_L is included: $R_{out} = R_C // R_L$, and

$$A_v = -\frac{R_C // R_L}{r_e'}$$

16

Overall Voltage Gain of CE Amplifier

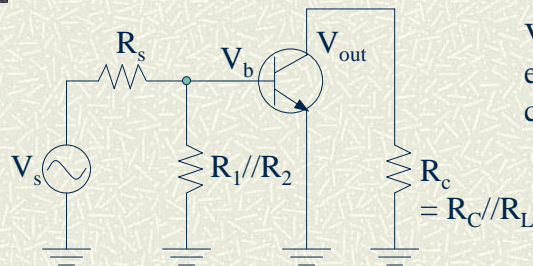

Voltage gain without emitter bypass capacitor, C_2 :

$$A_v = -\frac{R_c}{r_e' + R_E}$$


Rule of thumb on emitter bypass capacitor:

$$X_{C2} > R_E/10$$

$$A_v' = \frac{V_b}{V_s} A_v = \frac{R_{in(tot)}}{R_s + R_{in(tot)}} A_v$$

17

Stability of Voltage Gain

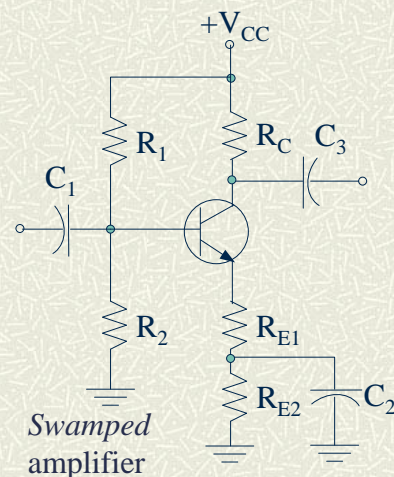

Bypassing R_E produces max. voltage gain but it is less stable since r_e' is dependent on I_E and temperature.


By choosing $R_{E1} > 10 r_e'$, the effect of r_e' is minimized without reducing the voltage gain too much:

$$A_v = -R_c/R_{E1}$$

$$R_{in(base)} = \beta_{ac}(r_e' + R_{E1})$$

18


Current Gain and Power Gain

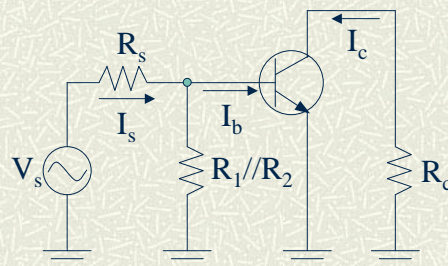

Base to collector current gain is β_{ac} but
 overall current gain is $A_i = I_c/I_s$ where $I_s = \frac{V_s}{R_{in(tot)} + R_s}$
 Overall power gain is: $A_p = A_v' A_i$

19

Common-Collector Amplifier

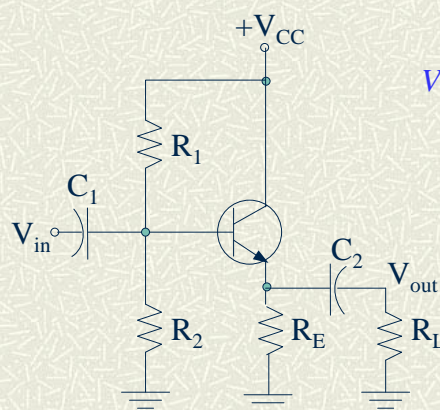

DC analysis:

$$V_B = \left(\frac{R_2 // \beta_{DC} R_E}{R_1 + R_2 // \beta_{DC} R_E} \right) V_{CC}$$

$$V_E = V_B - V_{BE}$$


$$I_E = V_E / R_E$$

$$V_C = V_{CC}$$

The CC amplifier is also known as an emitter-follower since V_{out} follows V_{in} in phase and voltage.

20

AC Analysis of CC Amplifier

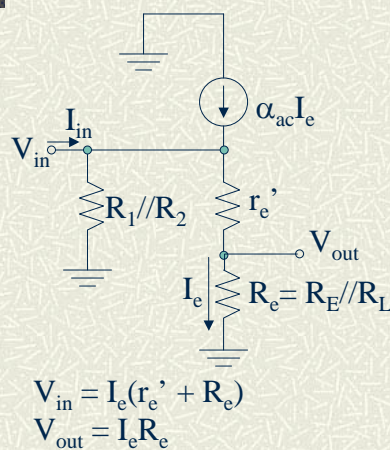

$$A_v = \frac{V_{out}}{V_{in}} = \frac{R_e}{(r_e' + R_e)}$$

$$R_{in(base)} \cong \beta_{ac}(r_e' + R_e)$$

If $R_e \gg r_e'$, then, $A_v = 1$,
and $R_{in(base)} = \beta_{ac} R_e$

$$R_{in(tot)} = R_1 // R_2 // R_{in(base)}$$


$$R_{out} = (R_s / \beta_{ac}) // R_e \text{ (very low)}$$

$$A_i = I_e / I_{in} = \beta_{ac} \text{ (if } R_1 // R_2 \gg \beta_{ac} R_e \text{)}$$

$$A_p = A_v A_i = A_i$$

21

Darlington Pair

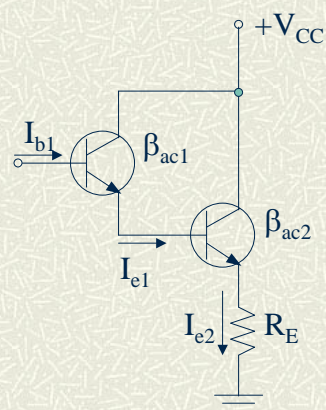

$$\# I_{e2} = \beta_{ac2} I_{e1} = \beta_{ac1} \beta_{ac2} I_{e1}$$

$$\# \text{ So, } \beta_{ac(overall)} = \beta_{ac1} \beta_{ac2}$$


Assuming $r_e' \ll R_E$,

$$R_{in} = \beta_{ac1} \beta_{ac2} R_E$$

Darlington pair has very high current gain, very high R_{in} , and very low R_{out} - ideal as a *buffer*

22

Common-Base Amplifier

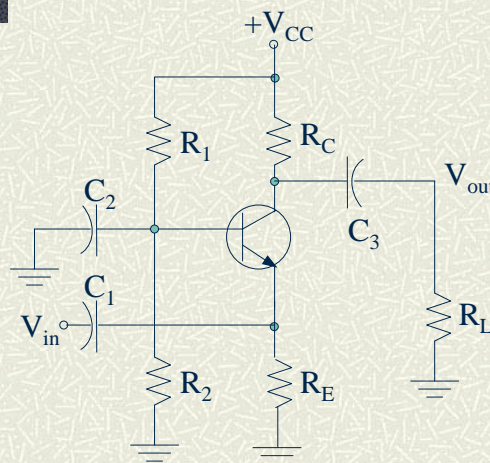


CB amplifier provides high A_v with a max. A_i of 1.

There is no phase inversion between V_{out} and V_{in} .

DC formulas are identical to those for CE amplifier.

23

AC Analysis of CB Amplifier

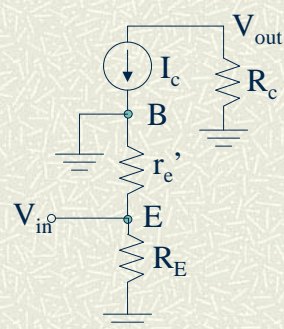

$$A_v = \frac{V_{out}}{V_{in}} = \frac{I_c R_c}{I_e (r_e' // R_E)} \cong \frac{R_c}{r_e' // R_E}$$

$$R_{in(emitter)} = r_e' // R_E$$

If $R_E \gg r_e'$, then

$$A_v \cong \frac{R_c}{r_e'}; R_{in(emitter)} = r_e'$$

$$R_{out} = R_c$$

$$A_i = 1; \text{ and } A_p = A_v$$


24

Comparing CE, CC, & CB Amplifiers

	CE	CC	CB
A_v	High ($-R_c/r_e'$)	Low ~ 1	High (R_c/r_e')
$A_{i(max)}$	High (β_{ac})	High (β_{ac})	Low ~ 1
A_p	Very high ($A_v A_i$)	High A_i	High A_v
$R_{in(max)}$	Low ($\beta_{ac} r_e'$)	High ($\beta_{ac} R_e$)	Very low (r_e')
R_{out}	High (R_c)	Very low ($R_s/\beta_{ac})/R_e$)	High (R_c)

25

Multistage Amplifiers

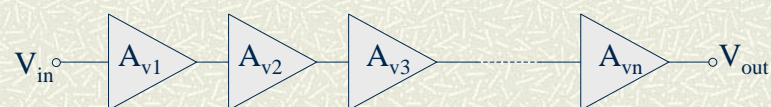


n amplifier stages in *cascade*

- Overall voltage gain, $A_{vT} = A_{v1} A_{v2} A_{v3} \dots A_{vn} = V_{out}/V_{in}$
- Overall gain in dB, $A_{vT(dB)} = A_{v1(dB)} + A_{v2(dB)} + \dots + A_{vn(dB)}$
where, $A_{v(dB)} = 20 \log A_v$
- The purpose of a multistage arrangement is to increase the overall voltage gain.

26


Two-stage CE Amplifier

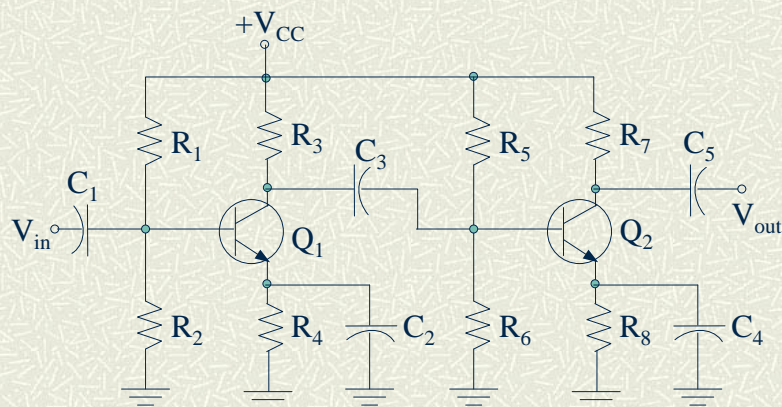

Capacitive coupling prevents change in dc bias

27

Analysis of 2-stage CE Amplifier

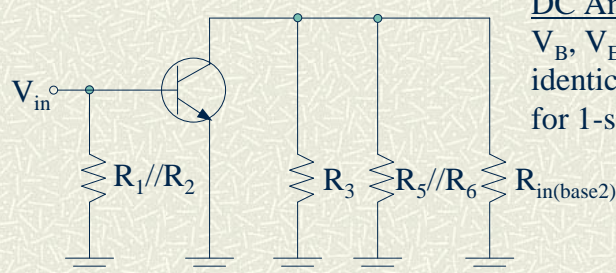

DC Analysis:

V_B , V_E , V_C and I_C are identical to those for 1-stage CE ampl.


AC Analysis:

$$R_{c1} = R_3 // R_5 // R_6 // R_{in(base2)}; A_{v1} = -\frac{R_{c1}}{r_e'}; A_{v2} = -\frac{R_{c2}}{r_e'} = -\frac{R_7}{r_e'}$$

$$A_{vT} = A_{v1} A_{v2}$$

28

2-stage Direct-Coupled Amplifier

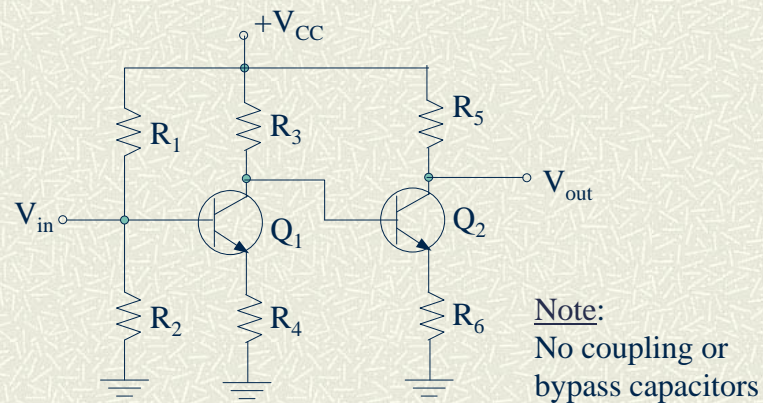


29

Notes on Direct-Coupled Amplifier

- # DC collector voltage of first stage provides base-bias voltage for second stage
- # Amplification down to 0 Hz is possible due to absence of capacitive reactances
- # Disadvantage - small changes in dc bias voltages due to temperature or power-supply variations are amplified by succeeding stages

30

Transformer-Coupled Multistage Amplifier

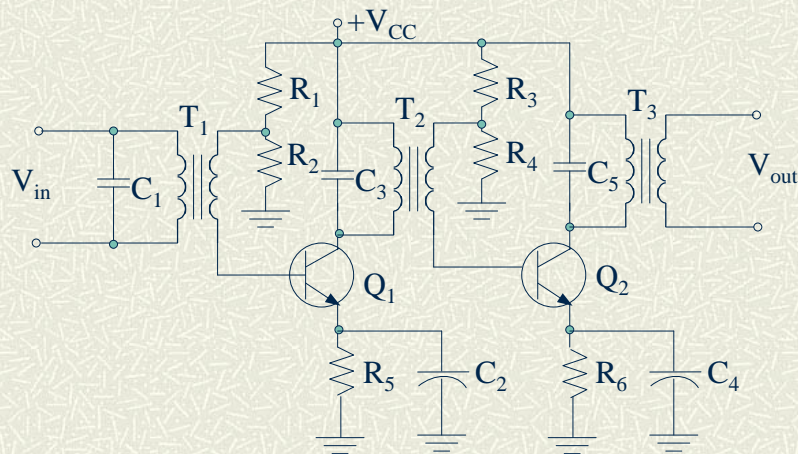

31

Notes On T'former-Coupled Amplifiers

- ✚ Transformer-coupling is often used in high-frequency amplifiers such as those in RF and IF sections of radio and TV receivers.
- ✚ Transformer size is usually prohibitive at low frequencies such as audio.
- ✚ Capacitors are usually connected across the primary windings of the transformers to obtain resonance and increase selectivity.

32

Typical Troubleshooting Process

- # Identify the symptom(s).
- # Perform a power check.
- # Perform a sensory check.
- # Apply a signal-tracing technique to isolate the fault to a single circuit.
- # Apply fault-analysis to isolate the fault further to a single component or group of components.
- # Use replacement or repair to fix the problem.

33

Power Amplifiers

- # Power amplifiers are large-signal amplifiers
- # They are normally used as the final stage of a communications receiver or transmitter to provide signal power to speakers or to a transmitting antenna.
- # Four classes of large-signal amplifiers will be covered: class A, class B, class AB, and class C.


34

Class A Amplifier Characteristics

- # Q-point is centred on ac load line.
- # Operates in linear region (i.e. no cutoff or saturation) for full 360° of input cycle.
- # Output voltage waveform has same shape as input waveform except amplified.
- # Can be either inverting or noninverting.
- # Maximum power efficiency is 25%.


35

Class A Operation: DC Load Line

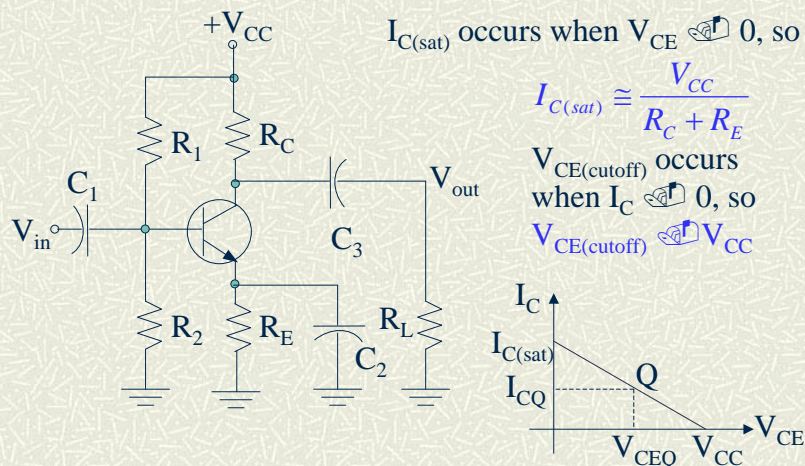

36

Class A Operation: AC Load Line

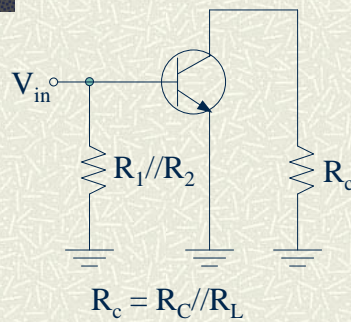

From Q-point to saturation point:


$$\Delta V_{ce} = V_{CEQ} ; \textcircled{8} \Delta I_c' = V_{CEQ} / R_c$$

$$I_{c(sat)} = I_{CQ} + \Delta I_c' = I_{CQ} + V_{CEQ} / R_c$$

From Q-point to cutoff point:


$$\Delta I_c = I_{CQ} ; \textcircled{8} \Delta V_{ce}' = I_{CQ} R_c$$
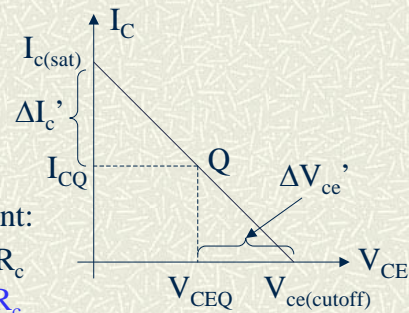
$$V_{ce(cutoff)} = V_{CEQ} + I_{CQ} R_c$$



37

Maximum Class A Operation

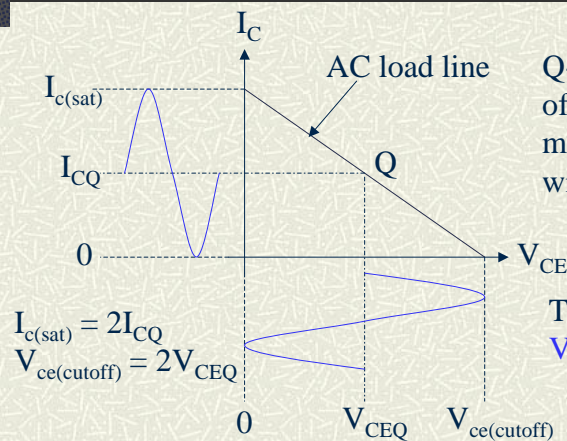


Q-point is at centre of ac load line for max. voltage swing with no clipping.

To centre Q-point:
 $V_{CEQ} = I_{CQ} R_c$

38

Non-linearity of r_e'

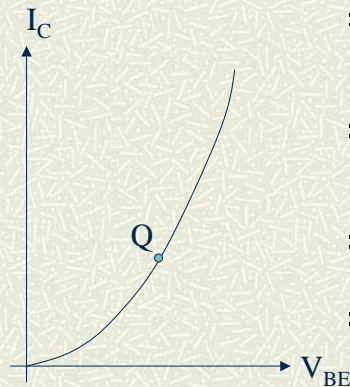

- # For large voltage swings, $r_e' \approx 25\text{mV}/I_E$ is not valid.
- # Instead, the average value of $r_e' = \Delta V_{BE}/\Delta I_C$ should be used for A_v formula.
- # Non-linearity of r_e' leads to distortion at output.
- # Reduce distortion by setting Q-point higher or use swamping resistor in the emitter.

39

Power & Efficiency: Class A Amplifier

- # Power gain, $A_p = A_i A_v \approx \beta_{DC} R_c / r_e'$
- # Quiescent power, $P_{DQ} = I_{CQ} V_{CEQ}$
- # Output power, $P_{out} = V_{ce} I_c = V_{out(rms)} I_{out(rms)}$
 - when Q-point is centred, $P_{out(max)} = 0.5 V_{CEQ} I_{CQ}$
- # Efficiency, $\eta = P_{out}/P_{DC} = P_{out}/(V_{CC} I_{CQ})$
- # When Q-point is centred, $\eta_{max} = 0.25$
- # Max. load power, $P_{L(max)} = 0.5 (V_{CEQ})^2 / R_L$


40

Class B Amplifier Characteristics

- # Biased at cutoff - it operates in the linear region for 180° and cutoff for 180°.
- # *Class AB* amplifier is biased to conduct slightly more than 180°.
- # Advantage of class B or class AB amplifier over class A amplifier - more efficient.
- # Disadvantage - more difficult to implement circuit for linear reproduction of input wave


41

Push-pull Class B Operation

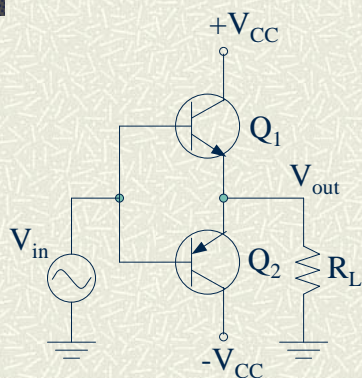


Complementary amplifier

An npn transistor and a matched pnp transistor form two emitter-followers that turn on alternately. Since there is no dc base bias, Q_1 and Q_2 will turn on only when $|V_{in}|$ is greater than V_{BE} . This leads to *crossover distortion*.

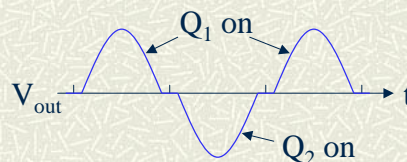

42


Class AB Operation

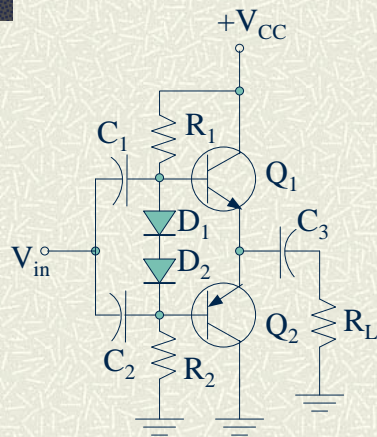

- # The push-pull circuit is biased slightly above cutoff to eliminate crossover distortion.
- # D_1 and D_2 have closely matched transconductance characteristics of the transistors to maintain a stable bias.
- # C_3 eliminates need for dual-polarity supplies.

43


Class AB Amplifier: DC Analysis

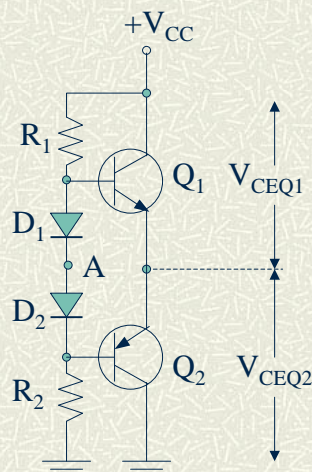

- # Pick $R_1 = R_2$, therefore $V_A = V_{CC}/2$
- # Assuming transconductance characteristics of diodes and transistors are identical, $V_{CEQ1} = V_{CEQ2} = V_{CC}/2$
- # $I_{CQ} \approx 0$ (cutoff)

44

Class AB Amplifier: AC Analysis

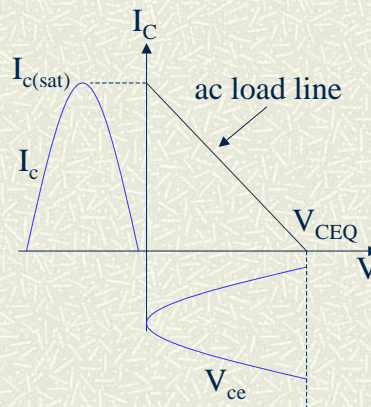

- # For max. output, Q_1 and Q_2 are alternately driven from near cutoff to near saturation.
- # V_{ce} of both Q_1 and Q_2 swings from $V_{ceQ} = V_{CC}/2$ to 0.
- # I_c swings from 0 to $I_{c(sat)} = V_{ceQ}/R_L$ $\Rightarrow I_{out(pk)}$
- # Input resistance, $R_{in} = \beta_{ac}(r_e' + R_L)$


45

Power & Efficiency: Class B Amplifier

- # Average output power, $P_{out} = V_{out(rms)} I_{out(rms)}$
- # For max. output power, $V_{out(rms)} = 0.707 V_{ceQ}$ and $I_{out(rms)} = 0.707 I_{c(sat)}$; therefore,
 $P_{out(max)} = 0.5 V_{ceQ} I_{c(sat)} = 0.25 V_{CC} I_{c(sat)}$
- # Since each transistor draws current for a half-cycle, dc input power, $P_{DC} = V_{CC} I_{c(sat)}/\pi$
- # Efficiency, $\eta_{max} = P_{out}/P_{DC} = 0.25\pi \Rightarrow 0.79$
- # The efficiency for class AB is slightly less.

46

Darlington Class AB Amplifier

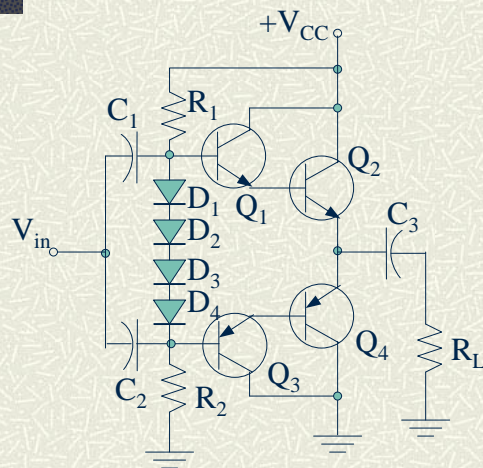

In applications where the load resistance is low, Darlington pairs are used to increase input resistance presented to driving amplifier and avoid reduction in A_v . 4 diodes are required to match the 4 base-emitter junctions of the darlington pairs.


47

Class C Amplifier Characteristics

- ⚡ Biased below cutoff, i.e. it conducts less than 180° .
- ⚡ More efficient than class A, or push-pull class B and class AB.
- ⚡ Due to severe distortion of output waveform, class C amplifiers are limited to applications as tuned amplifiers at radio frequencies (RF).


48

Basic Class C Operation

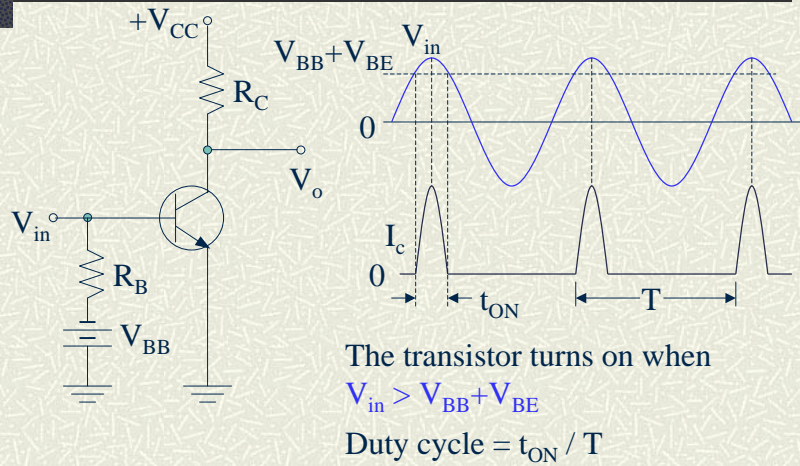

49

Tuned Operation

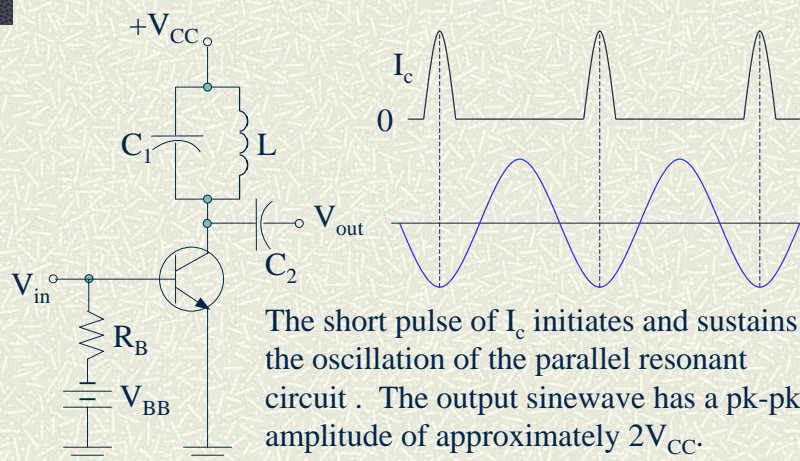

50

Power & Efficiency: Class C Amplifier

- Using simplification where current is $I_{C(sat)}$ and voltage is $V_{CE(sat)}$ at turn on, and assuming the entire load line is used, then

$$P_{D(avg)} = (t_{ON}/T)V_{CE(sat)}I_{C(sat)}$$


- Max. output power for tuned operation,

$$P_{out(max)} = (0.707V_{CC}^2) / R_c = 0.5 V_{CC}^2 / R_c$$

- Efficiency, $\eta = P_{out} / (P_{out} + P_{D(avg)})$
- When $P_{out} \gg P_{D(avg)}$, η approaches 100%.

51

Frequency Multiplier

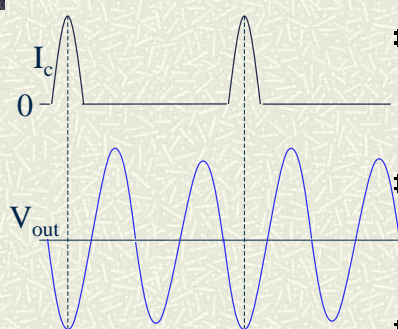


Output of tank circuit tuned to 2nd harmonic frequency

- Frequency “doubling” is obtained by tuning tank circuit to second harmonic of input frequency.
- By tuning tank circuit to higher harmonics, further frequency multiplication factors are achieved.
- Amplitude of each alternate peak drops due to energy loss in circuit.


52

Junction Field-Effect Transistor

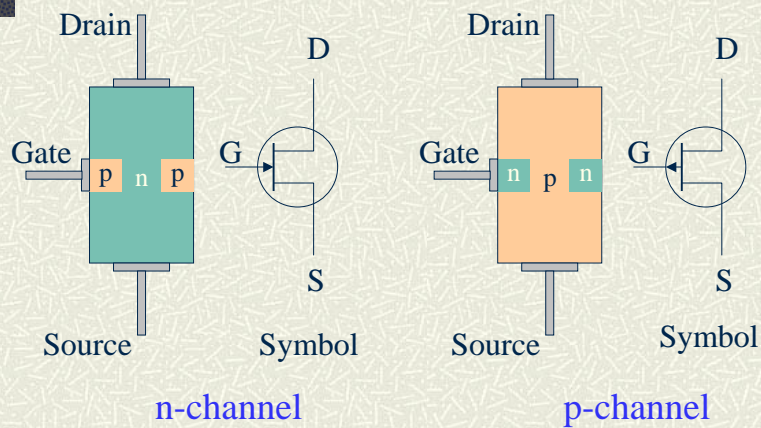

53

Basic Operation of JFET

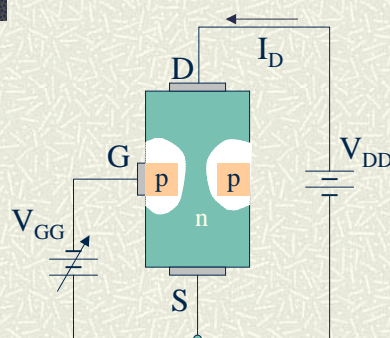


JFET is always operated with V_{GG} reverse-biased

- # Depletion region in n-channel increases its resistance.
- # Channel width and channel resistance can be controlled by varying V_{GG} (or V_{GS}), thereby controlling drain current, I_D .

54


JFET Characteristics For $V_{GS}=0$

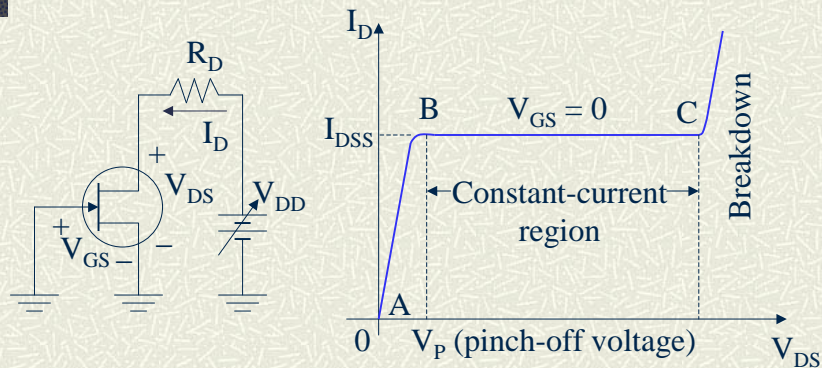

Between points A and B, $I_D \propto V_{DS}$ - ohmic region.
 I_{DSS} - max. I_D for a given JFET regardless of external circuit.

55


Controlling I_D With V_{GS}

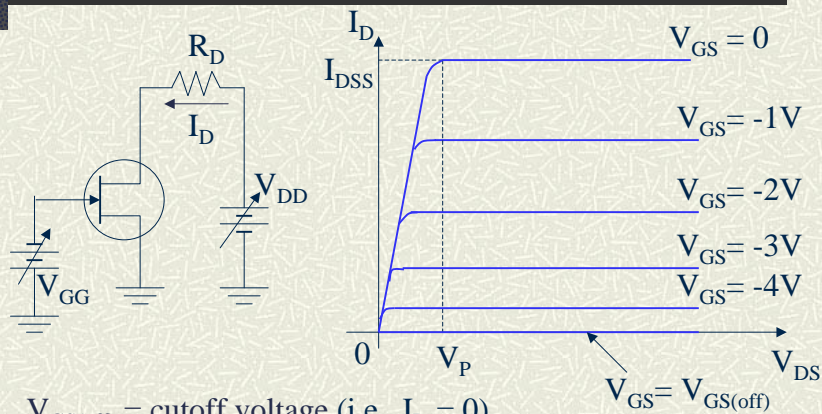

$V_{GS(off)}$ = cutoff voltage (i.e. $I_D = 0$)
 $V_{GS(off)} = -V_P$ (where V_P is measured at $V_{GS} = 0$)

56

JFET Transfer Characteristics

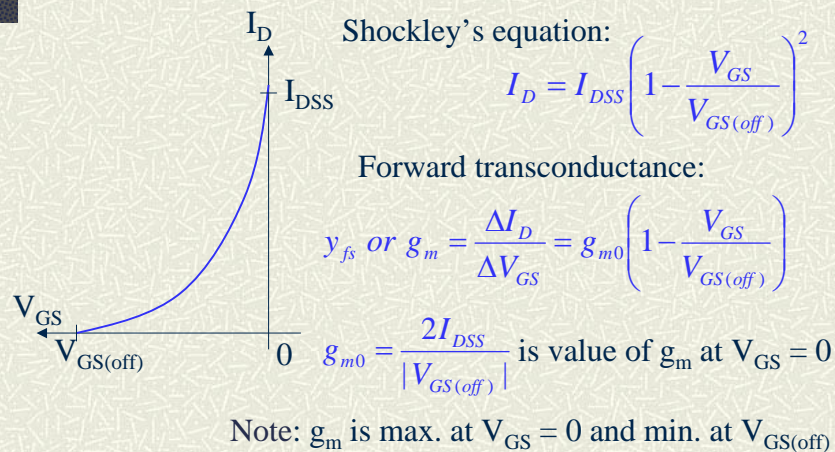


57

Other JFET Parameters

- ✚ JFET's input resistance, $R_{IN} = |V_{GS}/I_{GSS}|$ is very high since its gate-source junction is reverse-biased.
- ✚ Input capacitance, C_{iss} is typically a few pF.
- ✚ Output conductance, g_{os} , or output admittance, y_{os} , is typically 10 mS, and is the inverse of drain-to-source resistance, $r'_{ds} = \Delta V_{DS}/\Delta I_D$

58

JFET With Self-Biasing

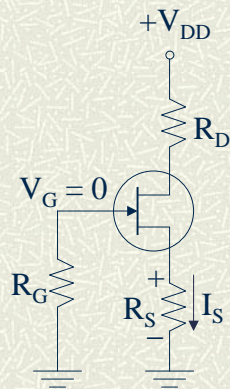

- # Large R_G is required to prevent shorting of input signal to ground and to prevent loading on the driving stage.
- # $V_{GS} = -I_D R_S$
- # $V_D = V_{DD} - I_D R_D$
- # $V_{DS} = V_D - V_S$
 $= V_{DD} - I_D (R_D + R_S)$

59


Setting Q-Point of JFET

- # First, determine I_D for a desired value of V_{GS} either by using transfer characteristic curve or Shockley's equation.
- # Then calculate $R_S = |V_{GS}/I_D|$
- # For midpoint bias (i.e. $I_D = 0.5 I_{DSS}$), make $V_{GS} \approx V_{GS(off)}/3.4$
- # To set $V_D = 0.5 V_{DD}$, pick $R_D = V_{DD}/(2I_D)$

60

Graphical Analysis of Self-Biased JFET

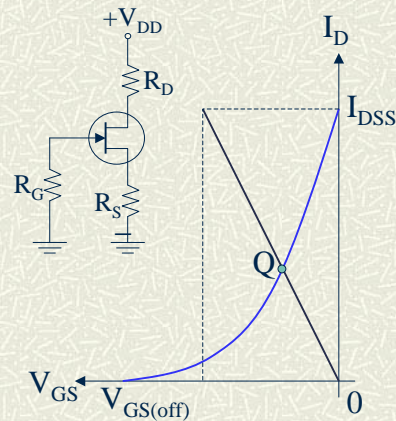- First obtain transfer characteristic curve from data sheet or plot using Shockley's equation.
- Draw dc load line by starting with $V_{GS} = 0$ when $I_D = 0$, and then $V_{GS} = -I_{DSS}R_S$ when $I_D = I_{DSS}$.



61

Voltage-Divider Bias


To keep the gate-source junction reverse-biased, $V_S > V_G$

$$V_S = I_D R_S$$

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD}$$


$$V_S = V_G - V_{GS}$$
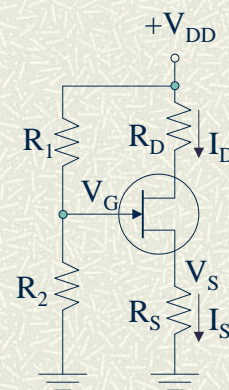
$$I_D = \frac{V_S}{R_S} = \frac{V_G - V_{GS}}{R_S}$$



62

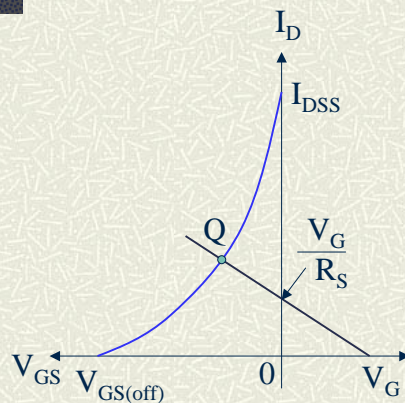Graphical Analysis of Voltage-Divider Biased JFET



For $I_D = 0$, $V_S = I_D R_S = 0$, and $V_{GS} = V_G - V_S = V_G$

For $V_{GS} = 0$,

$$I_D = \frac{V_G - V_{GS}}{R_S} = \frac{V_G}{R_S}$$

Draw the dc load line by joining the two points and extend it to intersect the curve to get the Q-point.

63

Q-Point Stability

- ✦ The transfer characteristic of a JFET can differ considerably from one device to another of the same type.
- ✦ This can cause a great variation of the Q-point, and consequently, I_D and V_{GS} .
- ✦ With voltage-divider bias, the dependency of I_D on the range of Q-points is reduced (i.e. more stable) because the slope is less than for self-bias, although V_{GS} varies quite a bit for both circuits.


64

Metal Oxide Semiconductor FET


- # The MOSFET differs from the JFET in that it has no *pn* junction structure.
- # The gate of the MOSFET is insulated from the channel by a silicon dioxide layer.
- # The two basic types of MOSFETs are depletion (D) and enhancement (E).
- # Because of the insulated gate, these devices are sometimes called IGFETs.

65

Depletion MOSFET

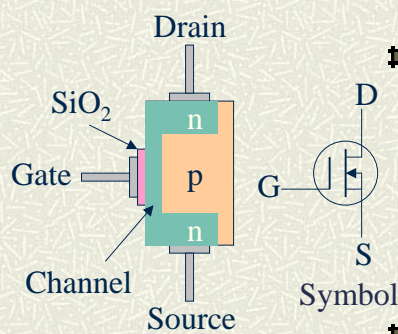

Basic structure of *n*-channel D-MOSFET

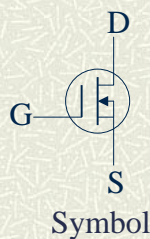

- # *n*-channel D-MOSFET is usually operated in the *depletion mode* with $V_{GS} < 0$ and in the *enhancement mode* with $V_{GS} > 0$.

- # *p*-channel D-MOSFET uses the opposite voltage polarity


66

Depletion/Enhancement MOSFET

- # Depletion Mode: negative gate voltage applied to n channel depletes channel of electrons, thus increasing its resistivity. At $V_{GS(off)}$, $I_D = 0$, just like n -channel JFET.
- # Enhancement mode: when $V_{GS} > 0$, electrons are attracted into channel, thus increasing (enhancing) the channel conductivity.

67

Enhancement MOSFET

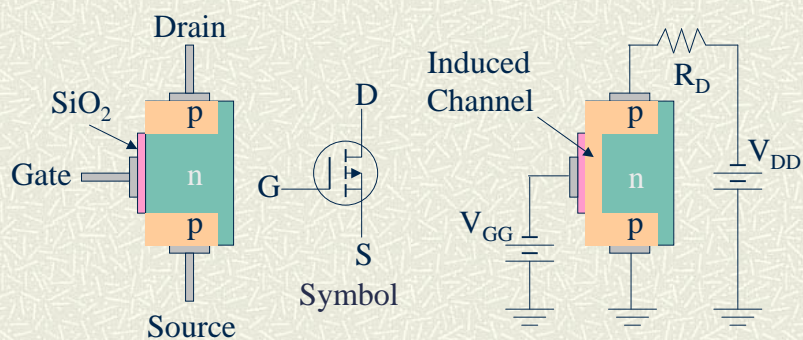

E-MOSFET construction and operation (p -channel)


68

Notes On E-MOSFET

- # The E-MOSFET operates *only* in the enhancement mode.
- # For a *p*-channel device, a negative gate voltage above a threshold value induces a channel by creating a layer of positive charges in the substrate region adjacent to the SiO_2 layer.
- # Channel conductivity increases with V_{GS} .

69

VMOS & TMOS Power MOSFETs

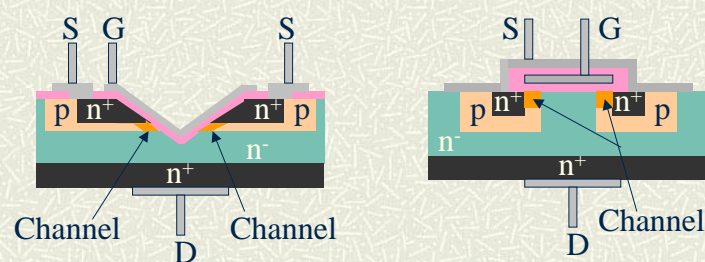


VMOS (V-groove MOSFET) creates a short and wide induced channel to allow for higher currents and greater power dissipation. Frequency response is also improved.

TMOS is similar to VMOS except it is easier to manufacture

70


D-MOSFET Transfer Characteristic

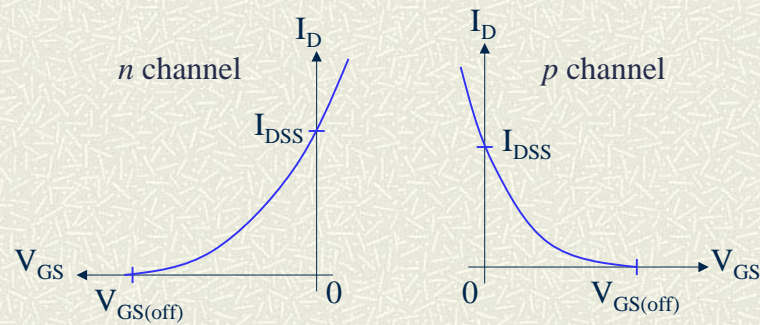

D-MOSFET can operate with either +ve or -ve gate voltage. Shockley's equation for the JFET curve also applies to the D-MOSFET curve.

71

E-MOSFET Transfer Characteristic

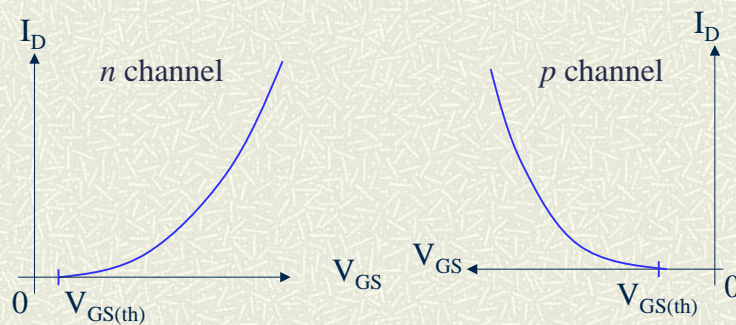

E-MOSFET uses only channel enhancement. Ideally $I_D = 0$ until $V_{GS} > V_{GS(th)}$. Transfer equation: $I_D = K(V_{GS} - V_{GS(th)})^2$, where K depends on the particular MOSFET.

72


MOSFET Handling Precautions



- # All MOS devices are subject to damage from *electrostatic discharge* (ESD).
- # To avoid damage from ESD:
 - ship/store MOS devices in conductive foam
 - ground all instruments and metal benches
 - ground assembler's/handler's body via resistor
 - never remove MOS device from live circuit
 - do not apply signals while dc supply is off

73


D-MOSFET With Zero-Bias

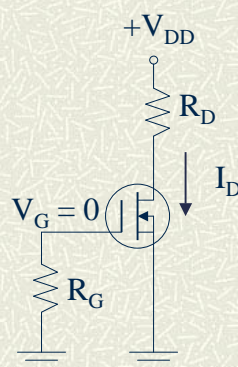

- # Since $V_{GS} = 0$, $I_D = I_{DSS}$.
- # $V_{DS} = V_{DD} - I_{DSS}R_D$
- # The value of R_G is chosen arbitrarily large to prevent loading of the previous stage and isolate any ac input signal from ground.

74

E- or D-MOSFET Bias

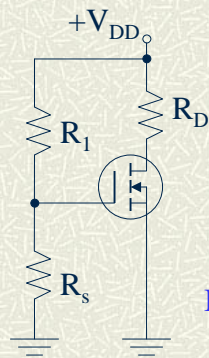


Voltage-divider bias

$$V_{GS} = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD}$$

$$V_{DS} = V_{DD} - I_D R_D$$

$$I_D = K(V_{GS} - V_{GS(th)})^2$$

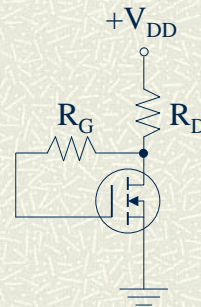


Drain-feedback bias


Since $I_G \approx 0$, $V_{GS} = V_{DS}$

75

Small-Signal JFET Amplifier

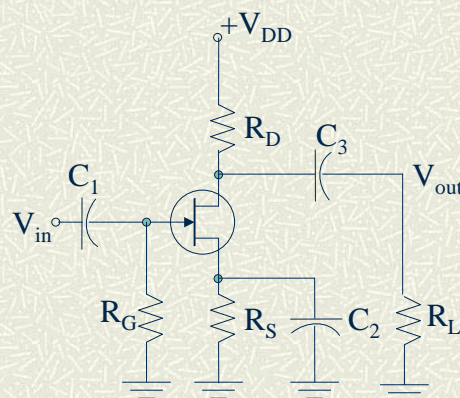


Common-source amplifier

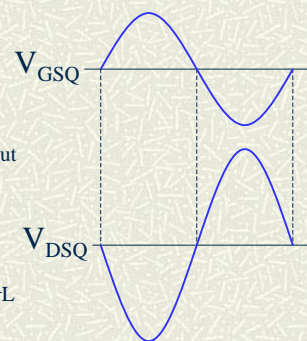

Voltage waveforms

76


JFET Transfer Characteristic Curve

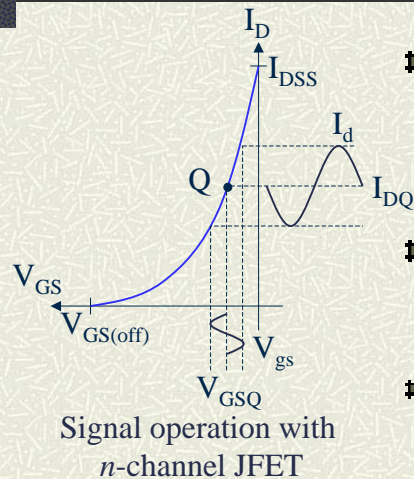

- # As V_{gs} swings from its Q-point to a more -ve value, I_d decreases from its Q-point.
- # When V_{gs} swings to a less -ve value, I_d increases.
- # Similar diagrams can be drawn for MOSFETs.

77

JFET Drain Characteristic Curve

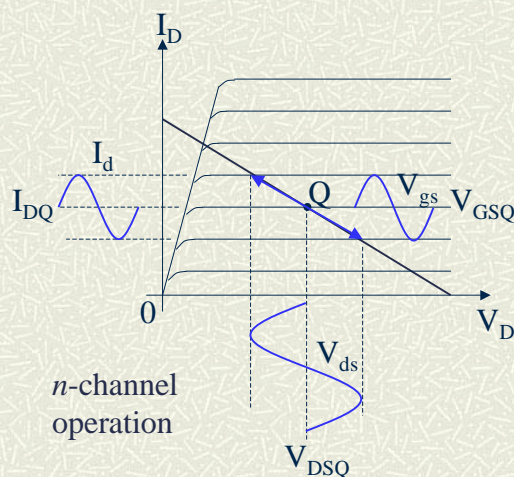


This is an alternative view of the JFET amplifier operation showing the variation of I_d with the corresponding change in V_{gs} & V_{ds} . Note that the CS amplifier is equivalent to the CE amplifier.

78


FET Simplified Equivalent Circuit

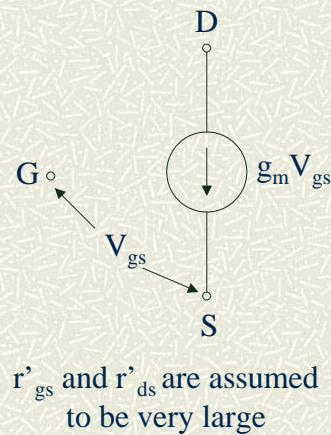- Transconductance is defined as $g_m = \Delta I_D / \Delta V_{GS}$ (siemens)
- In ac quantities, $g_m = I_d / V_{gs}$
- Rearranging the terms, $I_d = g_m V_{gs}$



79

DC Analysis of Common-Source Amplifier

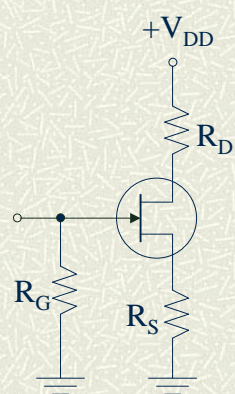

DC Equivalent circuit

If the circuit is biased at midpoint,

$$I_D = I_{DSS}/2$$

Otherwise, solve for I_D either graphically or by finding the root of the quadratic equation:


$$I_D = I_{DSS} \left(1 - \frac{I_D R_S}{|V_{GS(off)}|} \right)^2$$

where V_{GS} has been substituted by $I_D R_S$.

Then, $V_{DS} = V_D - V_S = V_{DD} - I_D(R_D + R_S)$

80

AC Analysis of CS Amplifier

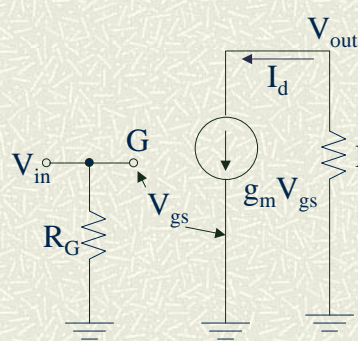

AC equivalent circuit

Since R_{in} is very high,

$$V_{gs} = V_{in}$$

$A_v = V_{out}/V_{in}$

$$= -I_d R_d / V_{gs} = -g_m R_d$$

where, $R_d = R_D // R_L$


$V_{out} = A_v V_{in}$

$$= -g_m R_d V_{in}$$

$$R_{in} = R_G // \left(\frac{V_{GS}}{I_{GSS}} \right)$$

81

Common-Source D-MOSFET Amplifier

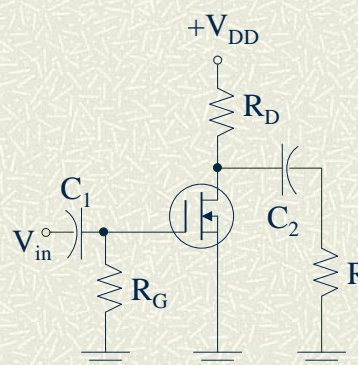

DC analysis is easier than for a JFET

because $I_D = I_{DSS}$ at $V_{GS} = 0$

Once I_D is known,


$$V_D = V_{DD} - I_D R_D$$

AC analysis is the same as for JFET

Thus, $A_v = -g_m R_d$

82

Common-Source E-MOSFET Amplifier

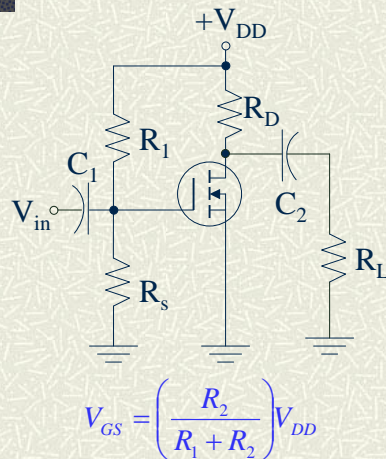

DC analysis:

$$\# I_D = K(V_{GS} - V_{GS(th)})^2$$

$$\# V_{DS} = V_{DD} - I_D R_D$$

AC analysis is same as JFET and D-MOSFET


$$\# \text{ i.e., } A_v = -g_m R_d$$

$$\# R_{in} = R_1 // R_2 // R_{IN(gate)}$$

$$\# R_{IN(gate)} = V_{GS} / I_{GSS}$$

83

Common-Drain Amplifier

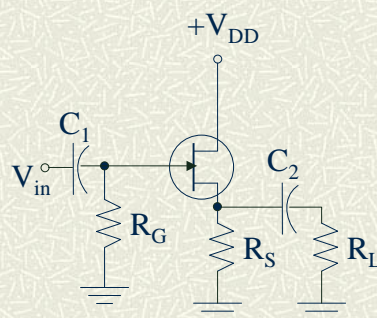

CD amplifier is comparable to the CC amplifier.

$$\# R_{in} = R_G // R_{IN(gate)}$$


$$\# V_{out} = I_d R_s = g_m V_{gs} R_s, \text{ where } R_s = R_s // R_L$$

$$\# V_{in} = V_{gs} + I_d R_s = V_{gs} + g_m V_{gs} R_s = V_{gs} (1 + g_m R_s)$$

$$\therefore A_v = \frac{V_{out}}{V_{in}} = \frac{g_m R_s}{1 + g_m R_s}$$

84

Common-Gate Amplifier

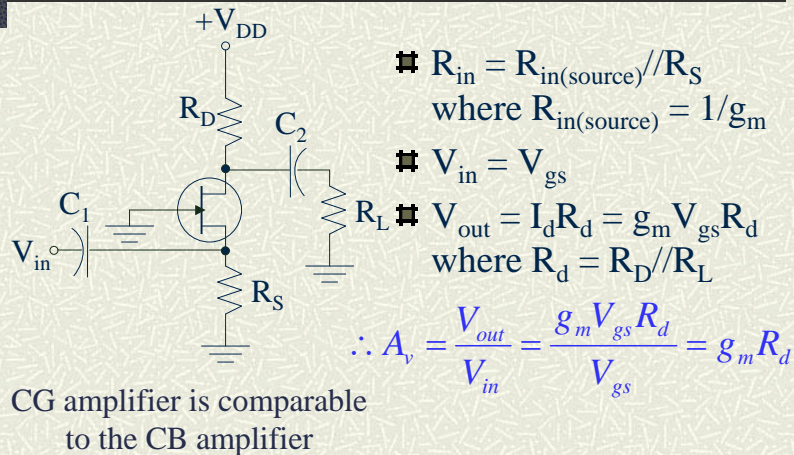

85

Amplifier Frequency Response

- # In the previous discussion of amplifiers, X_C of the coupling and bypass capacitors was assumed to be 0Ω at the signal frequency.
- # Also, the internal transistor capacitances were assumed to be negligible.
- # These capacitances, however, do affect the gain and phase shift of the amplifier over a specified range of input signal frequencies.


86

Effect At Low Frequency

- Since $X_C = 1/(2\pi fC)$, when f is low (e.g. <10 Hz), $X_C \gg 0$. The voltage drop across the input and output coupling capacitors become significant, leading to a drop in A_v . Also, a phase shift is introduced because the coupling capacitor form a *lead* (or RC) circuit at the input and the output.
- At low f , the significant X_C across R_E (or R_S) makes the emitter (or source) no longer at ground potential, again reducing A_v .

87

Effect At High Frequency

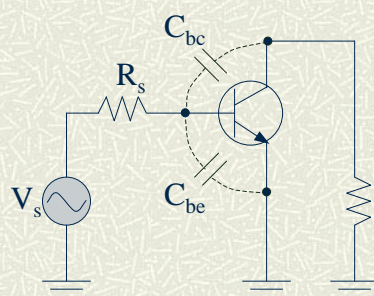


C_{bc} and C_{be} are internal junction capacitances which are usually a few pF.

- At high f , C_{be} causes a drop in signal voltage due to the voltage divider effect with R_s .
- At high f , C_{bc} allows negative feedback from output to cancel the input partially.
- A_v drops in each case.

88

General Frequency Response Curve

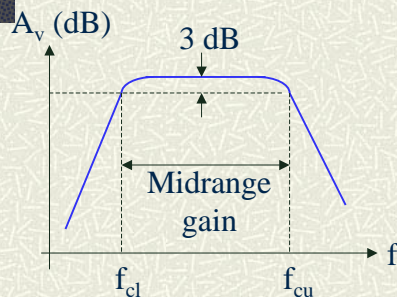


f_{cl} = lower cutoff frequency
 f_{cu} = upper cutoff frequency
 Gain is max. at midrange,
 often referenced as 0 dB.

- # $A_v \text{ (dB)} = 20 \log A_v$
- # Cutoff, critical, or corner frequency is the frequency when A_v or A_p drops by 3 dB. This corresponds to $0.707A_{v(\max)}$ or $0.5 A_{p(\max)}$ (half-power point) respectively.

89

Input RC Circuit At Low Frequency

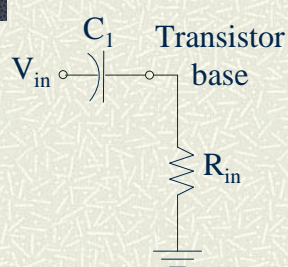

$$R_{in} = R_1 // R_2 // R_{in(\text{base})}$$

Critical frequency for this circuit is:


$$f_c = \frac{1}{2\pi R_{in} C_1}$$

$$V_{R(in)} \text{ leads } V_{in} \text{ by: } \theta = \tan^{-1} \left(\frac{X_{C1}}{R_{in}} \right)$$

Note: At f_c , $X_{C1} = R_{in}$, $\theta = 45^\circ$.


If R_s of input source is included:
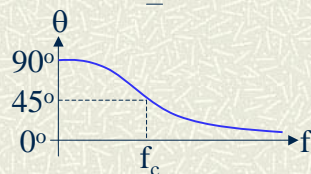
$$f_c = \frac{1}{2\pi (R_s + R_{in}) C_1}$$



90

Output RC Circuit At Low Frequency

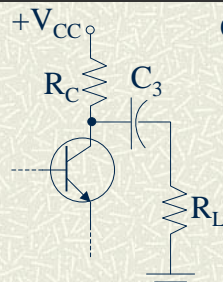


Critical frequency for the output RC circuit:

$$f_c = \frac{1}{2\pi (R_C + R_L) C_3}$$

The phase shift at the output:

$$\theta = \tan^{-1} \left(\frac{X_{C3}}{R_C + R_L} \right)$$

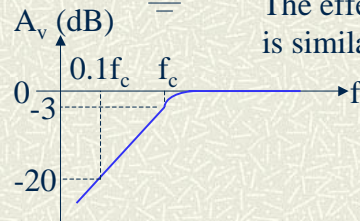
The effect of the output RC circuit on A_v is similar to that of the input RC circuit.



Drop in A_v for each RC circuit is **20 dB/decade** or **6 dB/octave**

91

Bypass RC Circuit At Low Frequency

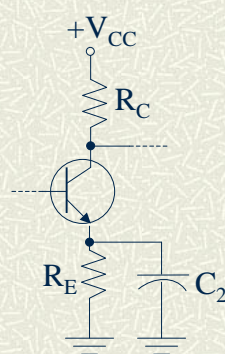

At low frequency, the impedance at the emitter is $Z_e = R_E // X_{C2}$, and A_v becomes:

$$A_v = \frac{R_C}{r'_e + Z_e}$$


The critical frequency is:

$$f_c = \frac{1}{2\pi [(r'_e + R_{th} / \beta_{ac}) // R_E] C_2}$$

where $R_{th} = R_1 // R_2 // R_s$ is the equivalent Thevenin resistance looking from the base toward the input source.

92

Total Low-Frequency Response

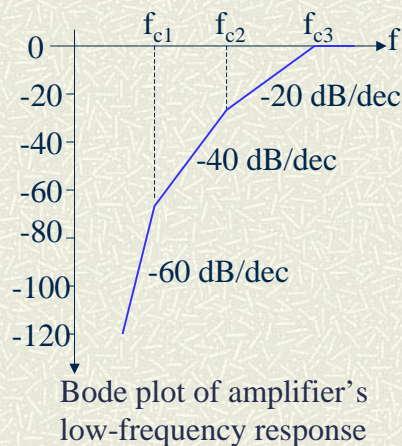

f_{c1} , f_{c2} , and f_{c3} are the critical frequencies of the bypass, output and input RC circuits (not necessarily in that order).

The RC circuit giving f_{c3} is known as the *dominant* RC circuit.

93


Direct-Coupled Amplifiers

- # Since direct-coupled amplifiers don't have coupling or bypass capacitors, their frequency response can extend down to dc.
- # Because of this, they are commonly used in linear ICs.
- # Although their gain is not as high as amplifiers with emitter bypass, A_v stays constant at lower frequencies.

94


Miller's Theorem

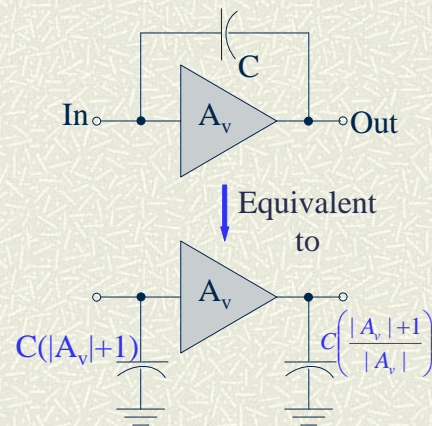- ✦ Miller's theorem can be used to simplify the analysis of inverting amplifiers at high frequencies.
- ✦ C in the diagram can represent either C_{bc} of a BJT or C_{gd} of a FET.



95

Input RC Circuit At High Frequency

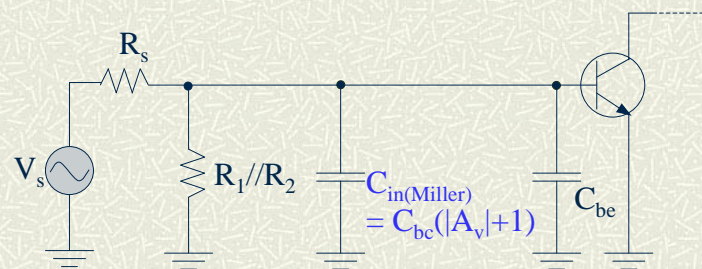

Critical frequency:

$$f_c = \frac{1}{2\pi R_{tot} C_{tot}}$$


Phase shift:

$$\theta = \tan^{-1} \left(\frac{R_{tot}}{X_{C(tot)}} \right)$$

where $R_{tot} = R_s // R_1 // R_2 // \beta_{ac} r'_e$; and $C_{tot} = C_{be} + C_{in(Miller)}$

96

Output RC Circuit At High Frequency

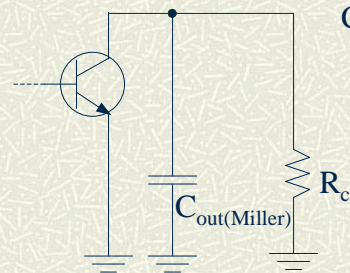

Critical frequency:

$$f_c = \frac{1}{2\pi R_c C_{out(Miller)}}$$

Phase shift:


$$\theta = \tan^{-1} \left(\frac{R_c}{X_{C_{out(Miller)}}} \right)$$

$$C_{out(Miller)} = C_{bc} \left(\frac{|A_v| + 1}{|A_v|} \right)$$

If $|A_v| \gg 10$, $C_{out(Miller)} \approx C_{bc}$

97


Total Amplifier Frequency Response

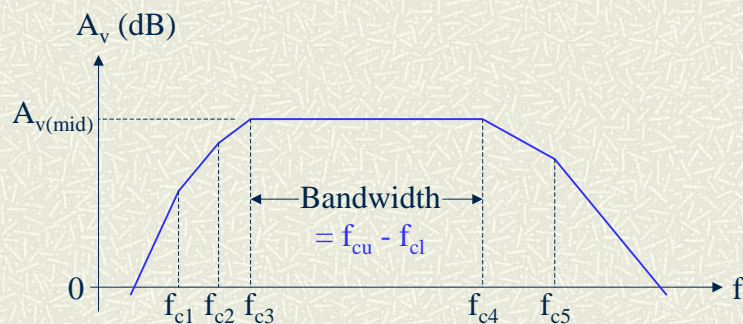

f_{c3} and f_{c4} are the two dominant critical frequencies where A_v is 3 dB below its midrange value. f_{c3} is the *lower cutoff frequency*, f_{cl} , and f_{c4} is the *upper cutoff frequency*, f_{cu} .

98


Gain-Bandwidth Product

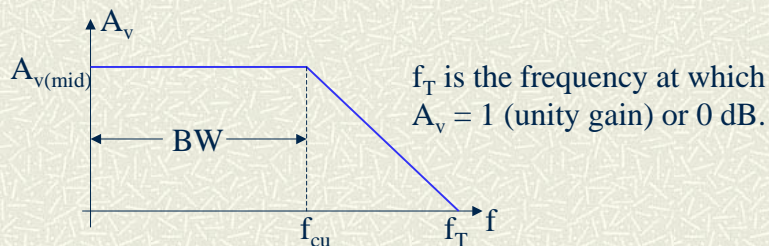

- # For a given amplifier, its *gain-bandwidth product* is a constant when the roll-off is -20 dB/dec.
- # If $f_{cu} \gg f_{cl}$, then $BW = f_{cu} - f_{cl} \approx f_{cu}$.
- # Unity-gain frequency, $f_T = A_{v(mid)} BW = A_{v(mid)} f_{cu}$.

99

FET Amplifier At Low Frequency

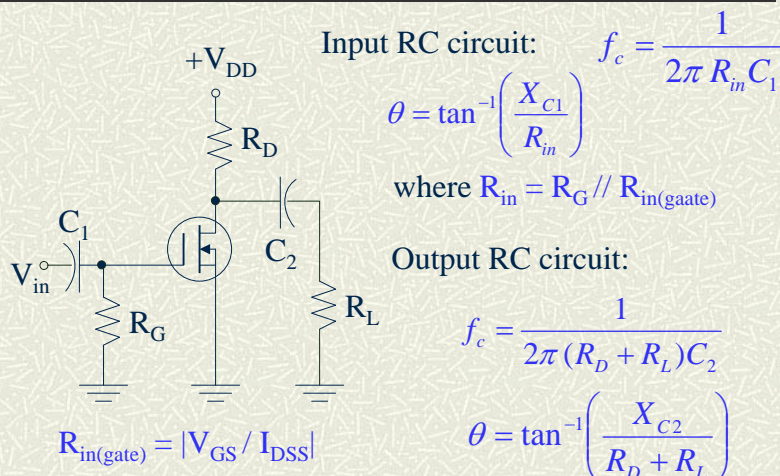

100

FET Amplifier At High Frequency

The high frequency analysis of an FET amplifier is very similar to that of a BJT amplifier. The basic differences are the specs of C_{gd} ($= C_{rss}$), and the determination of R_{in} .

Input RC circuit:
$$f_c = \frac{1}{2\pi R_s C_{tot}}; \theta = \tan^{-1} \left(\frac{R_s}{X_{C_{tot}}} \right)$$

where $C_{tot} = C_{gs} + C_{in(Miller)}$; $C_{in(Miller)} = C_{gd}(|A_v| + 1)$

Output RC circuit:

$$f_c = \frac{1}{2\pi R_d C_{out(Miller)}}; \theta = \tan^{-1} \left(\frac{R_d}{X_{C_{out(Miller)}}} \right); C_{out(Miller)} = C_{gd} \left(\frac{|A_v| + 1}{|A_v|} \right)$$

101

Multistage Amplifiers

For an amplifier formed by cascading several stages, the overall bandwidth is: $BW_{tot} = f'_{cu} - f'_{cl}$

If all the stages have the same f_{cl} and f_{cu} , then:

$$f'_{cl} = \frac{f_{cl}}{\sqrt{2^{1/n} - 1}} \quad \text{and} \quad f'_{cu} = f_{cu} \sqrt{2^{1/n} - 1}$$

If each stage has a different f_{cl} and a different f_{cu} , then f'_{cl} is determined by the stage with the highest f_{cl} , and f'_{cu} is determined by the stage with the lowest f_{cu} .

102